

TUTORIAL 14: DIRECT CURRENT CIRCUITS**Level 1 Solutions**




1	<p>Resistance for X = $(\frac{1}{2} + \frac{1}{4+3})^{-1} = 1.56 \Omega$</p> <p>Resistance for Y = $2 + (\frac{1}{4} + \frac{1}{3})^{-1} = 3.71 \Omega$ or $\frac{4 \times 3}{4+3} + 2$</p> <p>Resistance for Z = $(\frac{1}{3} + \frac{1}{2} + \frac{1}{4})^{-1} = 0.923 \Omega$</p> <p>Therefore, in order of increasing resistance is Z X Y.</p>	
4	<p>Method 1:</p> <p>Total R = $3 + (\frac{1}{6} + \frac{1}{6})^{-1} = 6.0 \Omega$</p> <p>$I = V / R = 12 / 6.0 = 2.0 \text{ A}$</p> <p>Hence the ammeter reading is 1 A.</p> <p>Method 2:</p> <p>$12 - I(3.0) = 0.5(I)(6.0) \rightarrow I = 2 \text{ A}$</p> <p>Hence the ammeter reading is 1 A.</p> <p>Note: The total current supplied by the battery will be split equally at the junction.</p>	
7	<p>Ans: B</p> <p>Let current flowing through R_1, R_2 and R_3 be i.</p> <p>$(R_1 + R_2 + R_3) i = 5 \text{ V} \quad (1)$</p> <p>$(R_2 + R_3) i = 3 \text{ V} \quad (2)$</p> <p>$(R_3) i = 2 \text{ V} \quad (3)$</p> <p>From (2) / (3), $\frac{R_2 + R_3}{R_3} = \frac{3}{2} \rightarrow \frac{R_2}{R_3} = \frac{1}{2}$</p> <p>Subst (2) into (1), $(R_1) i = 2 \text{ V} \rightarrow R_1 = R_3$</p>	
8	<p>Total R = $R + (\frac{1}{\frac{1}{R} + \frac{1}{R}})^{-1} = R + 0.5 R = 1.5 R$</p> <p>$V = \frac{0.5R}{1.5R} \times 6 = 2 \text{ V}$</p> <p>Hence the voltmeter reading is 2 V.</p>	<p>[1]</p> <p>[1]</p>
9	<p>Ans: D</p> <p>$\frac{2 \text{ k}\Omega}{2 \text{ k}\Omega + 4 \text{ k}\Omega} \times 12 \text{ V} = 4 \text{ V}$</p> <p>For Option A: $V_J = \frac{2 \text{ k}\Omega}{2 \text{ k}\Omega + 4 \text{ k}\Omega} \times 12 \text{ V} = 4 \text{ V}$</p> <p>For Option B: Diode is in reverse direction, therefore no current.</p> <p>For Option C: Diode is in reverse direction, therefore no current.</p> <p>$\frac{4 \text{ k}\Omega}{2 \text{ k}\Omega + 4 \text{ k}\Omega} \times 12 \text{ V} = 8 \text{ V}$</p> <p>For Option D: $V_J = \frac{4 \text{ k}\Omega}{2 \text{ k}\Omega + 4 \text{ k}\Omega} \times 12 \text{ V} = 8 \text{ V}$</p> <p>For Option E: Diode is in reverse direction, therefore no current.</p>	

14	$E_A = \frac{I_A}{I_S} E_S = \frac{66}{90} (15) = 11 \text{ V}$	[2]
----	---	-----


Level 2 Solutions

2	<p>When variable resistor is 0 kΩ, $R_c = 1.0 \text{ k}\Omega$.</p> <p>Voltmeter reading = 12 V (maximum)</p> <p>When variable resistor is 1.0 kΩ,</p> <p>Voltmeter reading = $\frac{1}{1 + (1 + 1)^{-1}} \times 12 = 8 \text{ V}$ (minimum)</p>	<p>[1]</p> <p>[1]</p> <p>[1]</p>
3(a)	<p>It is equivalent to the three branches in parallel (12 Ω, 6 Ω, 12 Ω),</p> <p>total resistance = $\left(\frac{1}{12} + \frac{1}{6} + \frac{1}{12} \right)^{-1} = 3 \Omega$</p>	[1]
(b)	<p>Consider resistor between AB to be in series to resistor between BC, resistance = 6 + 6 = 12 Ω.</p> <p>This will then be parallel the diagonal 6 Ω resistor,</p> <p>resistance = $\left(\frac{1}{12} + \frac{1}{6} \right)^{-1} = 4 \Omega$.</p> <p>This will then be in series to the 6 Ω resistor between CD, resistance will be 4 + 6 = 10 Ω.</p> <p>Finally, this is in parallel to the 6 Ω resistor between AD,</p> <p>resistance = $\left(\frac{1}{10} + \frac{1}{6} \right)^{-1} = 3.75 \Omega$.</p>	<p>[1]</p> <p>[1]</p> <p>[1]</p>
5	<p>Total $R = 20 + 50 + \left(\frac{1}{800} + \frac{1}{12000} \right)^{-1} = 820 \Omega$</p> <p>Ammeter reading, $I = \frac{6}{820} = 7.32 \text{ mA}$</p> <p>Voltmeter reading = $6 - (0.00732 \times 20) - (0.00732 \times 50) = 5.49 \text{ V}$</p>	<p>[1]</p> <p>[1]</p> <p>[1]</p>
6	<p>Ans: D</p> <p>When one or more filaments are broken, the circuit will be an open circuit and hence current is zero.</p> <p>PD across each of the <u>unbroken</u> filaments = $V = I R = (0)(R) = 0 \text{ V}$, where R is the resistance of each filament.</p> <p>Voltmeter Y thus reads <u>0 V</u>.</p> <p>For Voltmeter X, its left end is at the same potential as the left end of the 240 V supply (since there is no PD across the lamp on its left). The right end of Voltmeter X is at the same potential as the right end of the 240 V supply (since there is no PD across all the 4 lamps on its right!) Voltmeter X thus measures the PD across the <u>240 V supply</u>.</p>	

10	$V_{at Y} = \frac{R}{R + R_{LDR}} \times 6$ <p>When illuminated,</p> $2 = \frac{R}{R + 1200} \times 6$ $R = 600 \Omega$ <p>Note: When in the dark, resistance of LDR ($10 M\Omega$) is much bigger than resistance of R (600Ω). Therefore potential at Y will be approximately 0.</p>	
11 (a)(i)(1)	<p><u>Method 1: Potential Divider method</u></p> $\text{Voltage across LDR} = \frac{500}{30 + 500} \times 12 = 11.32 \text{ V}$ <p>Therefore,</p> $\text{Current through LDR} = \frac{11.32}{3000} = 3.77 \text{ mA}$ <p><u>Method 2:</u></p> $\text{Current supplied by battery} = \frac{12}{30 + 500} = 0.02264 \text{ A}$ $\text{Current supplied by battery} = \frac{12}{30 + 500} = 0.02264 \text{ A}$ $\text{Voltage across LDR} = 12 - (0.02264 \times 30) = 11.32 \text{ V}$ <p>Therefore,</p> $\text{Current through LDR} = \frac{11.32}{3000} = 3.77 \text{ mA}$	<p>[1]</p> <p>[1]</p> <p>[1]</p> <p>[1]</p>
(2)	$\text{Power dissipated in LDR} = 0.00377 \times 11.32 = 0.0427 \text{ W}$	[1]
(a)(ii)	<p>When R_{LDR} drops to 100Ω,</p> $\text{Current supplied by battery} = \frac{12}{30 + \left(\frac{1}{600} + \frac{1}{100} \right)^{-1}} = 0.1037 \text{ A}$ $\text{Voltage across LDR} = 12 - (0.1037 \times 30) = 8.889 \text{ V}$ $\text{Power dissipated in LDR} = \frac{8.889^2}{100} = 0.790 \text{ W} > 0.5 \text{ W}$	<p>[1]</p> <p>[1]</p>

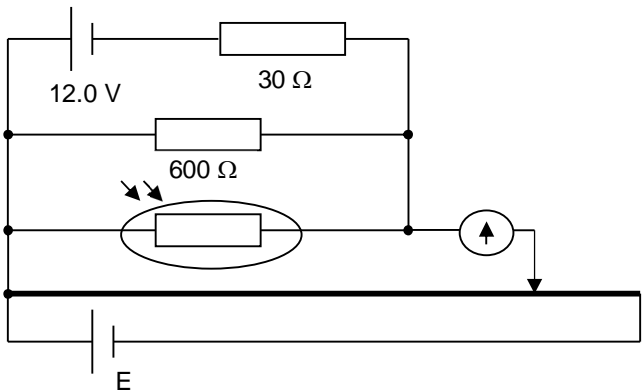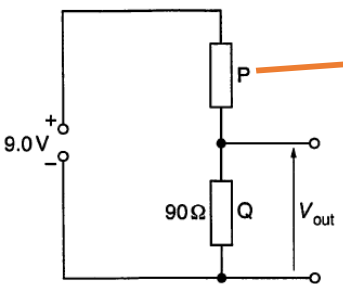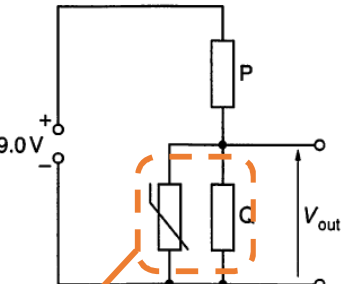	Hence, LDR will be overheated and damaged.	[1]
(b)	 <p>Note: Ensure that the polarity of E is correct as shown.</p>	[2]
12 (a)(i)	$V_{out} = I R_Q = 0.027 \times 90 = 2.43 \text{ V}$	[1]
(ii)	 <p>Step 1:</p> $R_P = \frac{(9.0 - 2.43)}{0.027} = 243.33 \Omega$  <p>Step 2:</p> <p>Combined parallel resistance = $\left(\frac{1}{120} + \frac{1}{90} \right)^{-1} = 51.43 \Omega$.</p> <p>Step 3:</p> <p>By potential divider rule,</p> $V_{out} = \frac{R_{//}}{R_{//} + R_P} \times 9.0 \text{ V}$ $= \frac{51.43}{51.43 + 243.33} \times 9 = 1.57 \text{ V}$	[1]
(iii)	When temp of thermistor increases, thermistor's resistance decreases. Thus the lower section's parallel combined resistance <u>decreases</u> , resulting in a decrease in the total circuit's resistance.	[1]

	<p>Since the emf remains the same, current delivered by battery <u>increases</u>.</p> <p>Thus the p.d. across resistor P <u>increases</u>, and by (Principle 2) $V_{\text{out}} = \text{emf} - V_P$, V_{out} thus <u>decreases</u>.</p>	<p>[1]</p> <p>[1]</p>
13 (b)(i)	<p>The variation of the resistance of the thermistor is much greater and more linear for temperature between 273 K to 293 than for temperature between 313 K to 333 K.</p> <p>Hence, the thermometer is more sensitive in the range 273 K to 293 K.</p>	<p>[1]</p> <p>[1]</p>
(ii)	$T = 292 \text{ K (approx.)}$	[1]
(c)(i)	$V_A = \frac{600}{600 + 400} \times 6 = 3.6 \text{ V}$ <p>For voltmeter to read 0 V, V_B has to be at 3.6 V as well.</p> <p>Hence,</p> $V_B = \frac{1200}{1200 + R_T} \times 6$ $3.6 = \frac{1200}{1200 + R_T} \times 6,$ $R_T = 800 \Omega$ <p>Therefore, $T = 305 \text{ K (from the graph)}$</p>	<p>[1]</p> <p>[1]</p> <p>[1]</p>
(ii)(1)	<p>When voltmeter read 1.2 V, it suggests that the voltage at point B could be either 1.2 V higher or lower than the voltage at A.</p> <p>Higher voltage at B will mean that the resistance of the thermistor is lower and hence the temperature is higher. Lower voltage will mean lower temperature.</p> <p>Hence the thermistor can be at 2 different temperatures.</p>	<p>[1]</p> <p>[1]</p>
(2)	$V_B = \frac{1200}{1200 + R_T} \times 6$ $3.6 \pm 1.2 = \frac{1200}{1200 + R_T} \times 6$ $4.8 = \frac{1200}{1200 + R_T} \times 6 \quad \text{OR} \quad 2.4 = \frac{1200}{1200 + R_T} \times 6$ $R_T = 300 \Omega \quad \text{OR} \quad R_T = 1800 \Omega$ $T = 333 \text{ K} \quad \text{OR} \quad T = 289 \text{ K}$ <p>Hence, the lower temperature will be 289 K.</p>	<p>[1]</p> <p>[1]</p> <p>[1]</p>


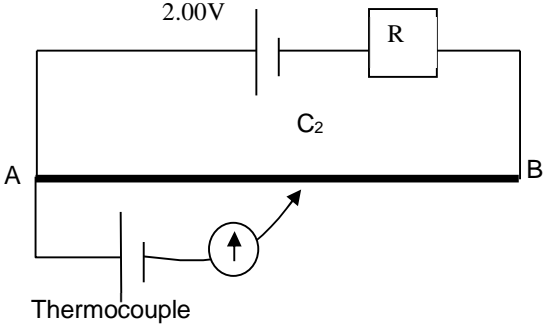
15	 <p> $V_{AC} = 4.00 \text{ mV}$, therefore $V_{AB} = 8.00 \text{ mV}$ $V_R = 2.00 - 0.008 = 1.992 \text{ V}$ $V_R = \frac{R}{R + 2.00} \times 2 = 1.992$ $R = 498 \Omega$ If $R' = 498 + 10 = 508 \Omega$ $V_{AB} = \frac{2}{2 + 508} \times 2 = 0.00784 \text{ V}$ $V_{AC} = \frac{L_{AC}}{L_{AB}} \times 7.84 \text{ mV} = 4.00 \text{ mV}$ Therefore $L_{AC} = 0.51 \text{ cm}$ The slider has to move 1 cm towards B. </p>	<p>[1]</p> <p>[1]</p> <p>[1]</p> <p>[1]</p>
16 (a)	<p>Potentiometer does not draw any current from the unknown emf when the balanced length is measured.</p> <p>whereas for a voltmeter, $V = E - I r$ and I is finite, hence, V will always show a reading lower than the true value.</p>	<p>[1]</p> <p>[1]</p>
(b) i	<p>By potential divider rule to lower /secondary circuit,</p> $V_{XZ} = \frac{100}{100+30} \times 2 \text{ V}$ $= 1.54 \text{ V}$	<p>[1]</p> <p>[1]</p>
ii	<p>Using V is proportional to L,</p> $\frac{L}{100 \text{ cm}} \times 4 \text{ V} = V_{XZ} = 1.54 \text{ V} \quad (\text{ans in (i)})$ $L = 38.5 \text{ cm}$	<p>[1]</p> <p>[1]</p>
iii	<p>Since there is no current in the secondary circuit when S_2 is closed and S_1 open,</p> <p>$V_{XZ} = \text{emf of secondary cell, } 2 \text{ V}$</p> $\frac{L}{100 \text{ cm}} \times 4 \text{ V} = V_{XZ} = 2 \text{ V}$ $L = 50.0 \text{ cm}$	<p>[1]</p> <p>[1]</p>
iv	<p>$I = 0$ at balance point (same as (iii), no current in the secondary circuit when S_2 is closed and S_1 open)</p>	<p>[1]</p>
v	<p>The fractional uncertainty is reduced when the balance length (XZ) measured is larger.</p>	<p>[1]</p>

	<p>This can be obtained when the potential across XY is lower by having another resistor connected in series with wire XY.</p> <p>Note that there is no internal resistance in driver cell! (as compared to lecture example 18.</p>	[1]
17(a)(i)	<p>Indicate on (1.5, 0.2) [draw a straight line from origin with gradient $1/(7.5) = 0.133$. The intersection with the graph is the answer]</p>	[1]
(ii)	<p>Max power = Max p.d. x max current = 4.5×0.36 = <u>1.6 W</u></p>	[1]
(b)	<p>As V increase, I increases and hence, temperature increases (as more electrical energy (IVt) is converted to thermal energy.)</p> <p>Amplitude of vibration of lattice ions increases and thus <u>collision frequency of electrons with lattice ions increases.</u></p> <p>Since the number of free electrons is fixed, there is <u>no increase in charge carriers.</u> Hence, <u>resistance increases with temperature.</u></p>	[1] [1] [1]
(c) (i)	<p>From the graph, when current is 0.36 A, p.d. across the lamp is 4.5 V (accept <u>4.45 to 4.55</u>)</p> <p>\therefore p.d. across 14Ω resistor = $(5.0 \times 0.36) + 4.5$ = 6.3 V (accept <u>6.25 to 6.35</u>)</p> <p>Current in the 14Ω resistor = $6.3 / 14 = \underline{0.45 \text{ A}}$ (allow ECF)</p>	[1] [1]
(ii)	<p>Current through battery = $0.36 + 0.45$ = <u>0.81 A</u> (allow ECF of 0.45A and/or 6.3V)</p> <p>Internal resistance $r = \frac{\text{p.d. across } r}{I} = \frac{7.5 - 6.3}{0.81} = \underline{1.5 \Omega}$</p>	[1] [1]
(d)(i)	<p>$V_{AB} = (12/15) \times 15 = \underline{12 \text{ V}}$</p> <p>$V_{AX} = (0.5/1.2) \times 12 = \underline{5 \text{ V}}$</p> <p>$E = V_{AX} = 5 \text{ V}$</p>	[1] [1]
(ii)	<p>The fractional error could be reduced by:</p> <ul style="list-style-type: none"> - using a resistance wire with smaller resistance per unit length/ smaller resistivity/ thicker wire. - add (an appropriate) resistor in series to the driver cell - decrease e.m.f. of driver cell <p>{1m for any one shown above}</p> <p>By potential divider rule, p.d. across resistance wire AB will decrease, hence length AX will increase and fractional error will be reduced.</p> <p>Do not accept increase of length of wire.</p>	[1] [1]


(iii)	V_{AY} = p.d across 4Ω resistor = $(4/5) \times 5 \text{ V}$ = <u>4 V</u> AY = $(4/12) \times 1.2 \text{ m}$ = <u>0.4 m</u>	 [1] [1]
-------	--	------------------------

- End of tutorial solutions -

Solutions to Additional Questions

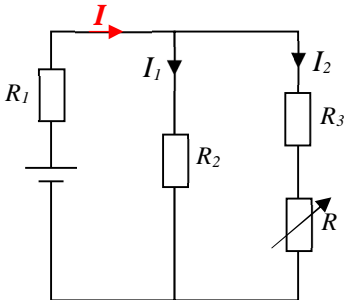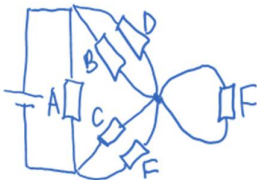1	<p>Answer: B</p> <p>Since R decreases, overall resistance of the circuit decrease. With the same EMF, the total current I will increase.</p>  <p>Therefore, the potential drop across R_1 increases. Therefore, the potential drop across R_2 ($\text{EMF} - V_{R1}$) decreases. Therefore, the current I_1 decreases.</p> <p>Since total current I will increase as discussed earlier, <u>therefore, I_2 must increase.</u></p>	
2	<p>Answer: C</p> <p>Since 1 filament breaks, therefore the parallel circuit is reduced by 1 branch. Hence, overall resistance increases (for parallel circuit in general, the more branches, the lower the resistance)</p> <p>Therefore, overall current decreases. Therefore, the potential drop across the internal resistor decreases. Therefore, the terminal p.d. (which is equal to the p.d. across each lamp) increases.</p> <p>Since, power = V^2/R, power delivered to each bulb has increased, brightness increases.</p>	
3	<p>Answer: B</p> <p>Effective resistance of B and D = effective resistance of C and E = $(10 \times 10)/(10 + 10) = 5.00 \, \Omega$</p> <p>Total effective resistance = $(\frac{1}{10} + \frac{1}{10})^{-1}$ = $5.00 \, \Omega$</p> <p>Current through cell = $V/I = 9.0 / 5.00 = 1.80 \, \text{A}$</p> 	



4

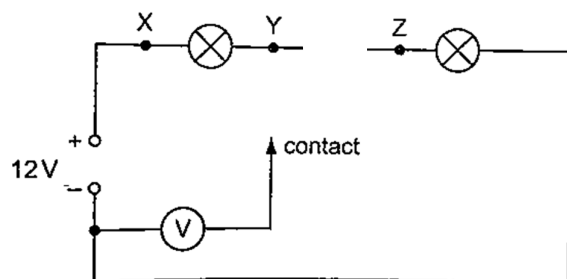Answer: C


Since bulb L has a broken filament, the circuit is broken and no current flows. Hence,

- No pd across X and Y. Potential at $Y = X =$ potential at +ve terminal.
- Therefore, p.d. reading at $X = 12\text{ V} =$ p.d. reading at Y
- Since no current flows, potential $Z =$ potential at -ve terminal. Therefore, p.d. reading at $Z = 0\text{ V}$.


5

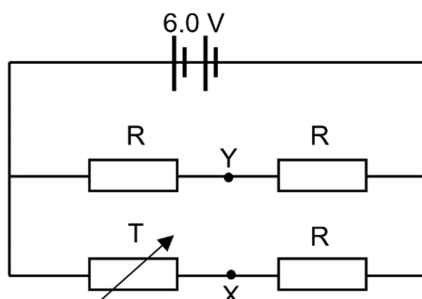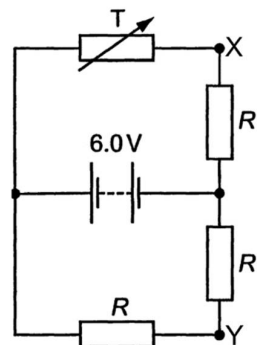Answer: B

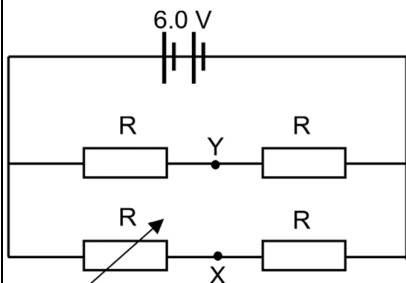It is easier to solve the question by removing the voltmeter and just keep in mind that we are looking at p.d. between X and Y. After that, we can redraw the circuit such that it make it easier for us to understand the circuit (on the right).







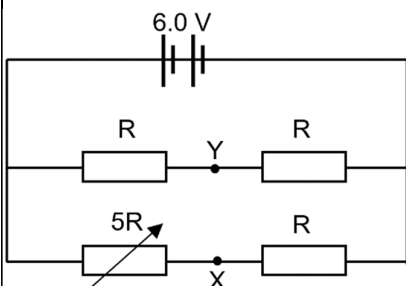
When $T = R$, p.d. across X and Y = 0
(since p.d. between +ve terminal to Y =
p.d between +ve terminal to X = 3.0 V)



- When $T = 5R$,
- p.d. across +ve to Y = 3.0 V
 - p.d. across +ve to X = $\frac{5}{6} \times 6 = 5.0\text{ V}$

Hence, p.d. across X and Y when T varies from R to 5 R is $5.0 - 3.0 = 2.0\text{ V}$

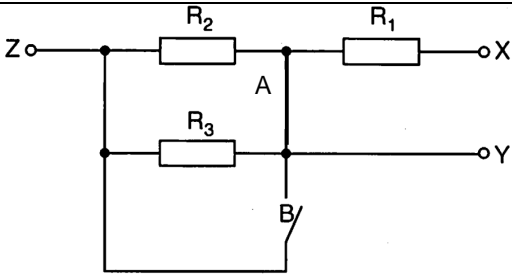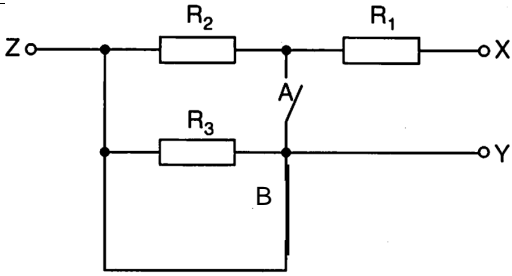6	<p>Answer: C</p> <p>Resistance of 1 branch of N resistors in series = NR</p> <p>Resistance of N branch in parallel = $(1/NR + \dots + 1/NR)^{-1}$</p> $= (N / NR)^{-1}$ $= R$	
7	<p>From the first circuit, $V_{BC} = 1.5 \text{ V}$ and $V_{BD} = \frac{R_{BD}}{R_{BD} + 1.0} \times 2.0$</p> <p>At balance length,</p> $0.9375 \times V_{BD} = 1.5$ $0.9375 \times \frac{R_{BD}}{R_{BD} + 1.0} \times 2.0 = 1.5$ $R_{BD} = 4.0 \Omega$ <p>From the second circuit, to balance at point D, then</p> $V_{BD} = 1.0 / 1.5 \times 1.5$ $\frac{4.0}{4.0 + 1.0 + R} \times 2.0 = 1.0$ <p>Solving,</p> $R = 3.0 \Omega$	<p>[1]</p> <p>[1]</p> <p>[1]</p> <p>[1]</p>
8(ai)	 <p>When A is closed and B is open, effective resistance between X & Y = $R_1 = 6 \Omega$ since there is a short circuit that allows current to bypass R_2 and R_3 and goes straight to Y.</p> <p>Therefore, $R_1 = 6 \Omega$</p>	
(ii)	 <p>When A is open and B is closed, effective resistance between X & Y = $R_1 + R_2 = 10 \Omega$ since there is a short circuit that allows current to bypass R_3.</p> <p>Therefore, $R_2 = 4 \Omega$</p>	

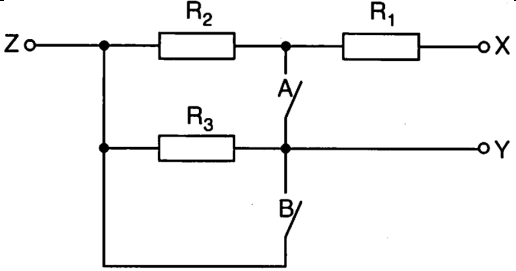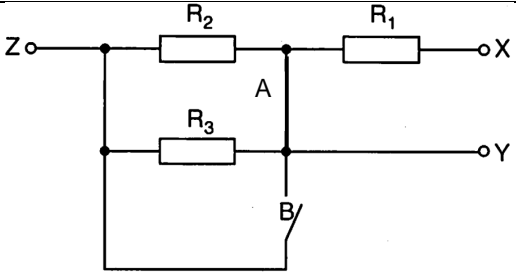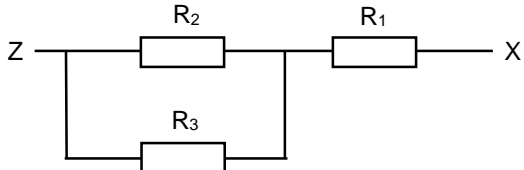(iii)	 <p>When both A and B are open, effective resistance between X & Y = $R_1 + R_2 + R_3 = 12\ \Omega$ since the current has to flow through all 3 resistors to reach Y. Therefore, $R_3 = 2\ \Omega$</p>	
(b)	 <p>When A is closed and B is open, the above is the actual circuit.</p> <p>The circuit can be redrawn as below:</p>  <p>R_2 is parallel to R_3, and their effective resistance is in series with R_1. Hence, resistance between Z and X = $(1/4 + 1/2)^{-1} + 6 = 7.33\ \Omega$</p>	